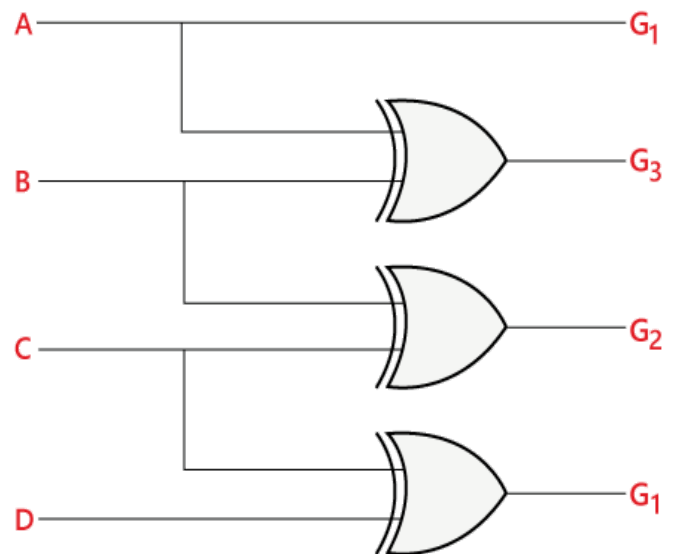


- Design a BCD to Gray code converter.

BCD Input				Gray Output			
B ₀	B ₁	B ₂	B ₃	G ₀	G ₁	G ₂	G ₃
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1



- What are the fundamental properties of Boolean algebra?

Boolean algebra is a mathematical structure essential for understanding logic, digital circuits, and computer science. Here are the key properties:

- Identity Laws
 - AND Identity: $A \cdot 1 = A$
 - OR Identity: $A + 0 = A$
- Null Laws
 - AND Null Law: $A \cdot 0 = 0$
 - OR Null Law: $A + 1 = 1$
- Idempotent Laws
 - $A \cdot A = A$
 - $A + A = A$
- Complement Laws
 - $A \cdot A' = 0$
 - $A + A' = 1$
- De Morgan's Theorems
 - $(A \cdot B)' = A' + B'$
 - $(A + B)' = A' \cdot B'$
- Double Negation Law
 - $A'' = A$

- What is meant by isomorphic Boolean algebra?

Isomorphic Boolean algebras refer to two Boolean algebras that are structurally identical in the sense that there is a one-to-one correspondence between their elements that preserves the algebra's operations.


- What is a synchroniser?

A synchroniser is a digital circuit or device used in electronics and digital systems to ensure that signals or data transferred between different clock domains are aligned properly.


- Design a sequence detector for 1X1X with overlap.

- Draw and explain the 4-bit Linear Feedback Shift Register.

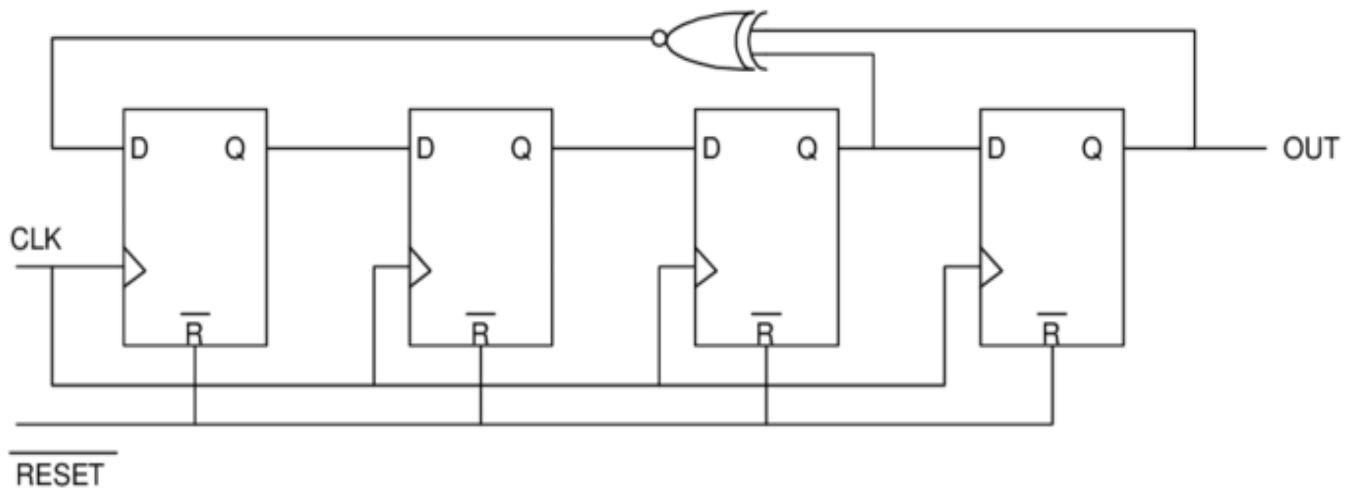A 4-bit Linear Feedback Shift Register (LFSR) is a sequential shift register that uses linear feedback to produce a sequence of binary values that appear random. It is often used in applications like pseudo-random number generation, cryptography, and digital circuits for testing and verification.



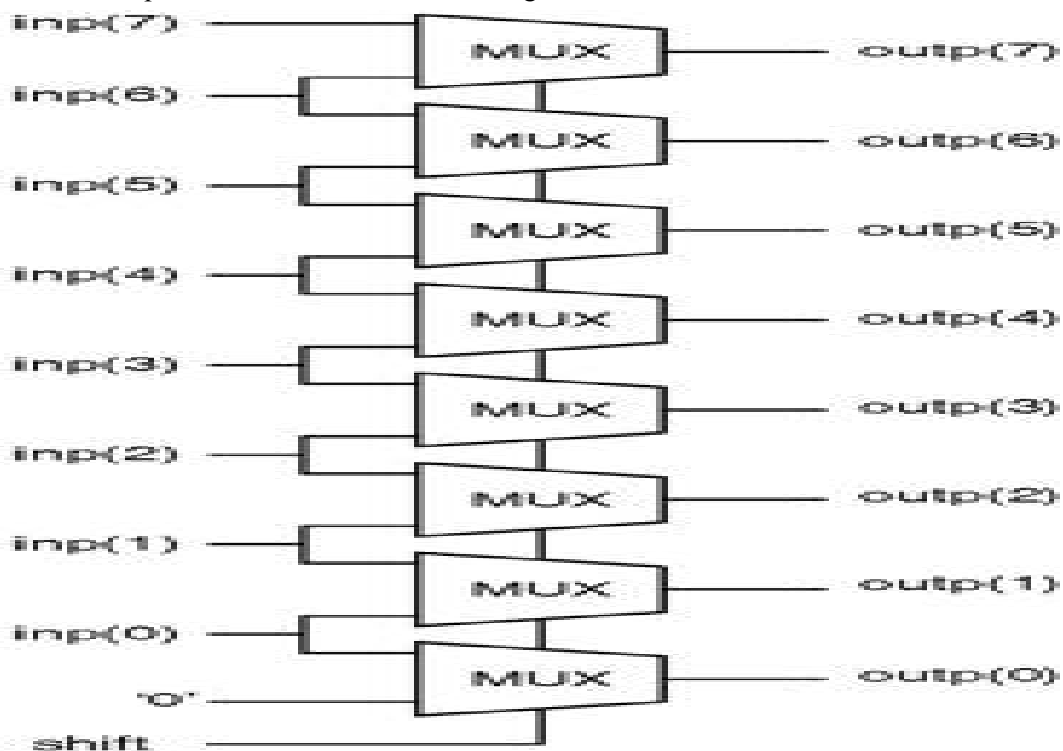7. Draw and explain the 4-bit barrel shifter using MUX



A 4-bit Barrel Shifter is a combinational circuit that can rotate or shift a 4-bit data input left or right by a specified number of positions. A barrel shifter can perform the shift in one clock cycle and is often implemented using multiplexers (MUXes).

8. Design a PISO Shift register?

